

MARANDA 2025 KCSE PREDICTION



EXPECTED EXAM 1



ELECTRICITY

448/1

PAPER 1 (Theory)

TIME: 2½ HOURS

NAME.....

SCHOOL..... SIGN.....

INDEX NO..... ADM NO.....

Kenya Certificate of Secondary Education.

INSTRUCTIONS TO CANDIDATES

- a) Write your **Name**, **Index number** and **Class** in spaces provided
- b) Candidates should have the following for this examination
Drawing instruments
Scientific calculator
- c) This paper consists of two sections: **A** and **B**.
- d) Attempt **ALL** questions in **section A** and any **FOUR** in **section B**.
- e) All dimensions are in **millimeters** unless stated other wise

For Examiner's use only

Section	Questions	Maximum Score	Candidate's Score
A	1-10	48	
B	11	13	
	12	13	
	13	13	
	14	13	

	15	13	
--	----	----	--

SECTION A (48 marks)

(Attempt all questions in this section)

1. Explain the significance of using only one hand when working on high voltage system

(2 marks)

.....

.....

.....

2. a) Define each of the following terms:

(3 marks)

i. semiconductor

.....

.....

ii. intrinsic semiconductor

.....

.....

iii. extrinsic semiconductor

.....

.....

b) Draw and label voltage versus current characteristics curve for a P-N junction in its forward and reverse modes

(3 marks)

3. a) A $5\text{k}\Omega$ linear potentiometer has 6V source connected across its end terminals

- i. Determine the range of output voltage of the potentiometer (1 mark)

.....

.....

.....

- ii. Calculate the two possible output voltages when the potentiometer is in its three-quarter position (2 marks)

.....

.....

.....

- b) An emf of 120V causes a current of 3A to flow in a circuit. Calculate the energy supplied by the source in 12 seconds (2 marks)

.....

.....

.....

.....

4. a) Outline two differences between a permanent magnet and an electromagnet (2 marks)

.....

.....

.....

.....

- b) State and explain two properties of a good conductor (2 marks)

.....

.....

.....

.....

5. a) List four electrical measurements that can be taken using a cathode ray oscilloscope
(2 marks)

.....
.....
.....
.....

b) A moving coil meter gives a full scale deflection for a current of 100mA and has a resistance of 5Ω.
Determine the value of the resistor used so that the meter can measure a current of 1.0A at full scale deflection.
(3 marks)

.....
.....
.....
.....
.....

6. a) Draw the current discharge curve of a capacitor (2 marks)

b) Outline how insulation resistance test can be carried out between two conductors (5 marks)

.....
.....
.....
.....
.....
.....

7. a) Name the logic gate shown in **Figure 1** (1 mark)

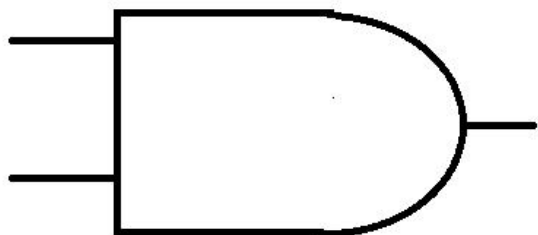


Figure 1

Name.....

b) Complete the truth table of the OR gate (2 marks)

INPUT 1	INPUT 2	OUTPUT
0	0	
0	1	
1	0	
1	1	

c) Perform each of the following number conversions (4 marks)

i. 101010_2 to decimal

.....

.....

.....

ii. 23_{10} to binary

.....

.....

.....

8. a) Name four sources of electricity in Kenya (2 marks)

.....

.....

.....

.....

b) State one possible cause and remedy for each of the following electric motor faults

(4 marks)

i. Motor connected to the supply but will not start

.....

.....

.....

ii. Motor overheats on load

.....

.....

.....

9. Draw wiring diagram of a 12V electric bell controlled by two switches from a 240V mains supply

(4 marks)

10. a) Define entrepreneur

(1 mark)

.....

.....

b) List two business opportunities in the field of electricity

(1 mark)

.....

.....

.....

SECTION B (52 marks)

*Answer any **four** questions from this section in the spaces provided*

11.a) State three variables which determine resonance condition in an RLC circuit **(3 marks)**

b) A series circuit consisting of a $0.1\mu\text{F}$ capacitor and a $25\mu\text{H}$, 20Ω coil is connected across a 10V a.c supply. Calculate the following: **(10 marks)**

- i. Resonant frequency
- ii. Supply current at resonance
- iii. Voltage across the capacitor at resonance

12. With the aid of a labelled diagram, show the construction and describe the operation of a moving coil permanent magnet type instrument **(13 marks)**

13.a) Explain the term ideal transformer **(3 marks)**


b) A transformer which has a primary winding resistance of 1Ω and a secondary winding resistance of 0.1Ω is connected to a 10Ω load. if the primary current is 0.5A and secondary is 5A , calculate:

(6 marks)

- i. Load power
- ii. Copper losses
- c) If the transformer in (b) has a core loss of 5W , calculate the efficiency of the transformer

(4 marks)

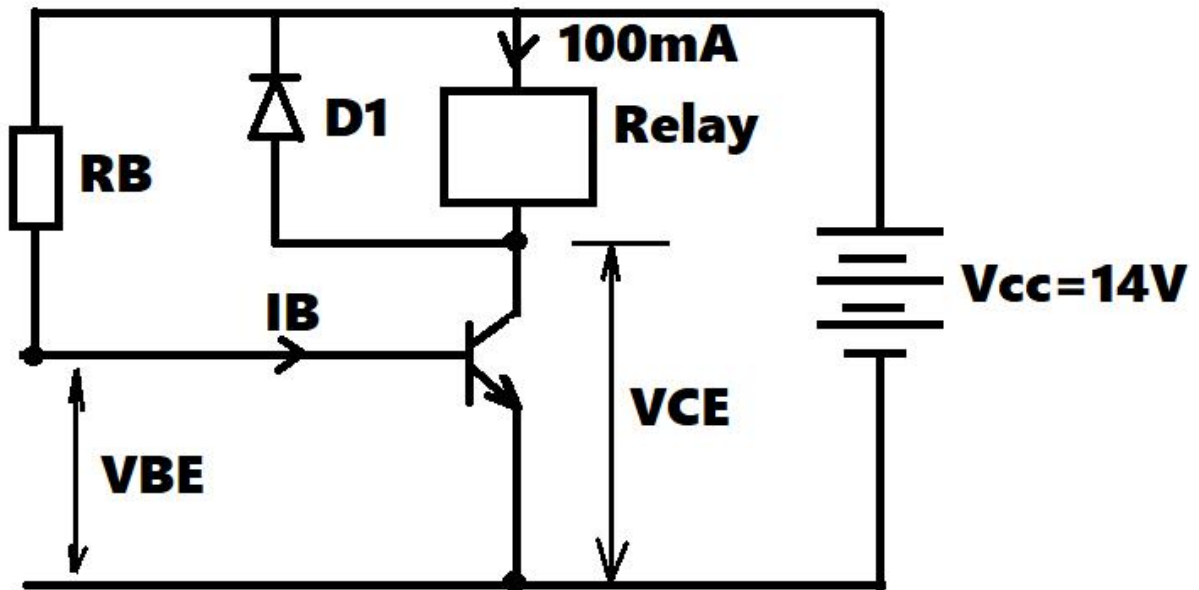14. The transistor in the circuit shown in **Figure 2** below is biased to supply the relay with 100mA . the dc current gain, β , of the transistor is 50 and the forward base-emitter voltage, V_{BE} is 0.7V



- a. If the voltage drop across the relay is 12V, calculate the: (11 marks)
- Base current I_B
 - Emitter current I_E
 - Voltage between collector and emitter V_{CE}
 - The base resistance R_B
- b. Explain the function of diode $D1$ in the circuit (2 marks)

15. Figure 3 shows three views of an object drawn in first angle orthographic projection. make isometric drawing of the object taking A as the closest point (13 marks)

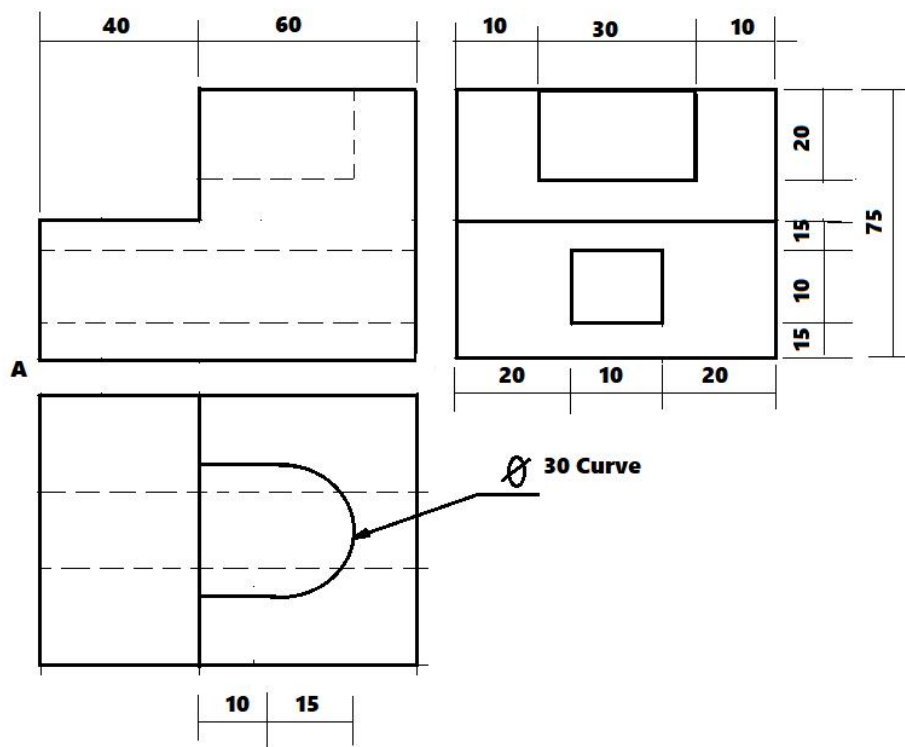


Figure 3