

MARANDA 2025 KCSE PREDICTION



EXPECTED EXAM 1



ELECTRICITY

448/2

PAPER 2 (Practical)

TIME: 2½ HOURS

NAME.....

SCHOOL..... SIGN.....

INDEX NO..... ADM NO.....

Kenya Certificate of Secondary Education.

INSTRUCTIONS TO CANDIDATES

- Write your **Name**, **Class** and **Index Number** in spaces provided
- There are **five** exercises in this examination
- Candidates are allowed **30** minutes for each exercise
- Each exercise will be awarded a maximum of 20 marks
- At each station, candidates are **not allowed** to either view the previous station's work or read instructions for the other stations
- Attempt all the **four** exercises
- All dimensions are in **millimeters** unless otherwise stated
- Candidates should answer the questions in **English**

For examiner's Use only

EXERCISE	1	2	3	4	TOTAL
MARKS(EC)					
MARKS(MC)					
GRAND TOTAL					

EXERCISE 1

Using the materials, equipment and measuring instruments provided, perform the following tasks

- a) Connect the circuit as shown in **Figure 1** ($2\frac{1}{2}$ marks)

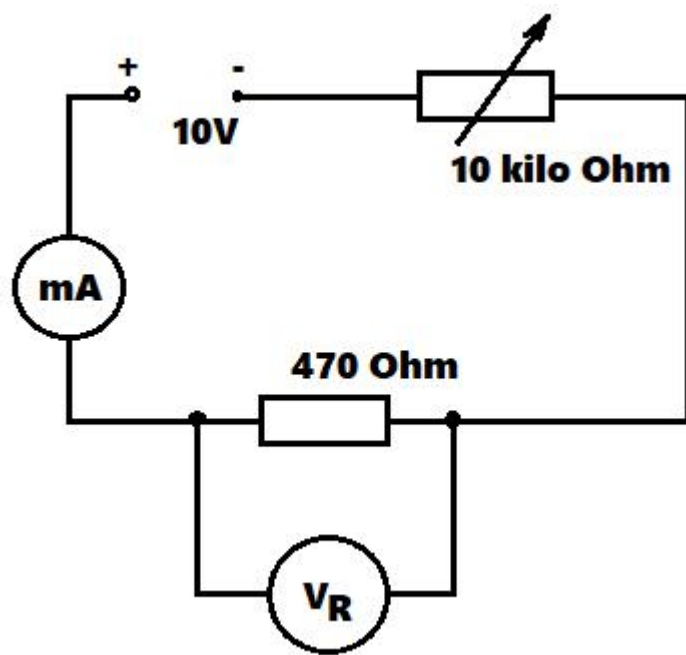


Figure 1.


- b) Connect the circuit to the power supply (1 marks)
- c) Turn the power on and adjust the potentiometer to obtain each of the voltages (V_R) shown in **Table 1**.in each case read and record the corresponding current I. (6 marks)

V_R (Volts)	I(mA)	Power (mW)
3		
4		
5		
6		
7		
8		

- d) For each value of V_R , calculate the power dissipated in the 470Ω resistor and complete the table (5 marks)
- e) Using the values in **Table 1** draw the graph of power against voltage V_R . ($5\frac{1}{2}$ marks)

EXERCISE 2

Using tools equipment and materials provided make the space bar saddle as shown in Figure 2

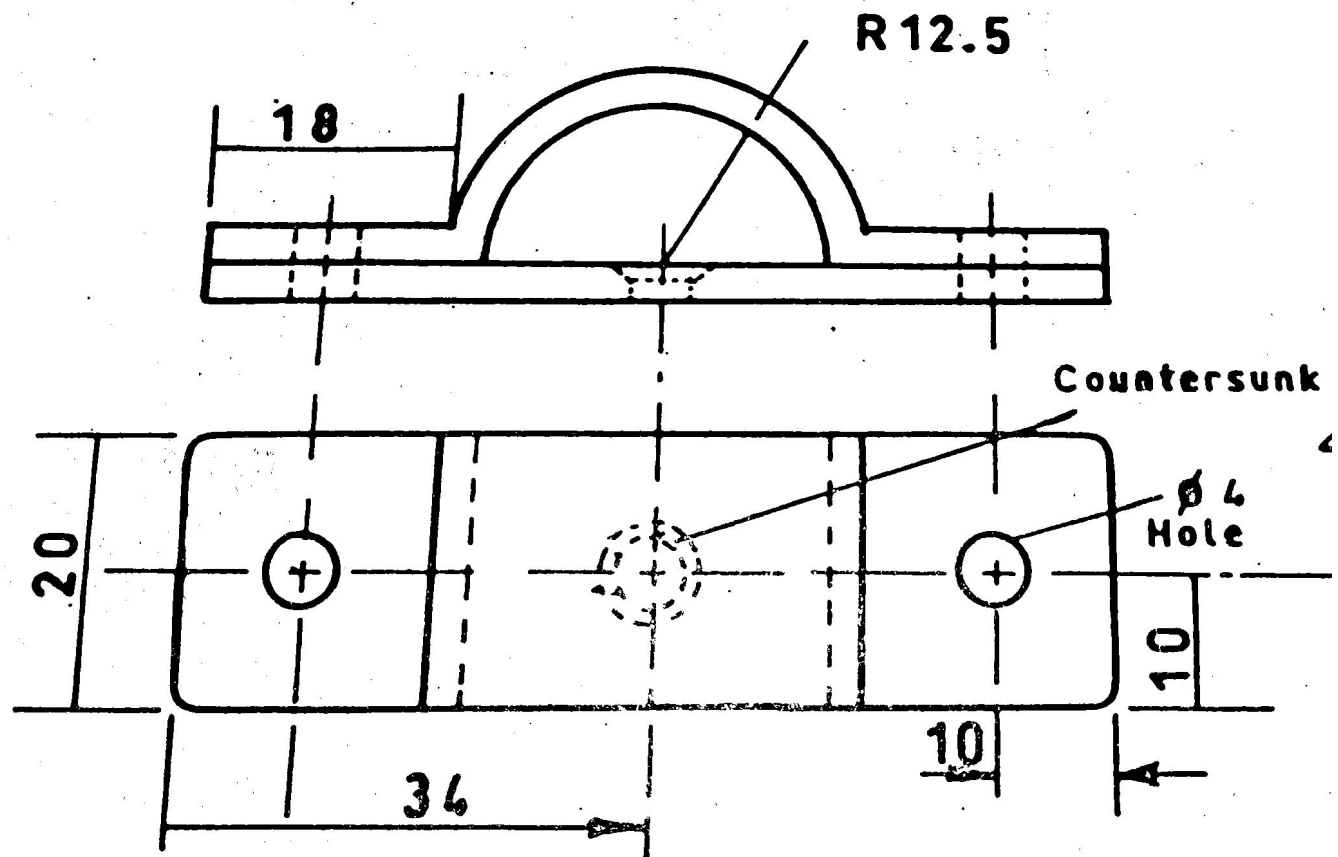

EXERCISE 3

a. Connect circuit as shown in figure 3. Let examiner check your work (2 marks)

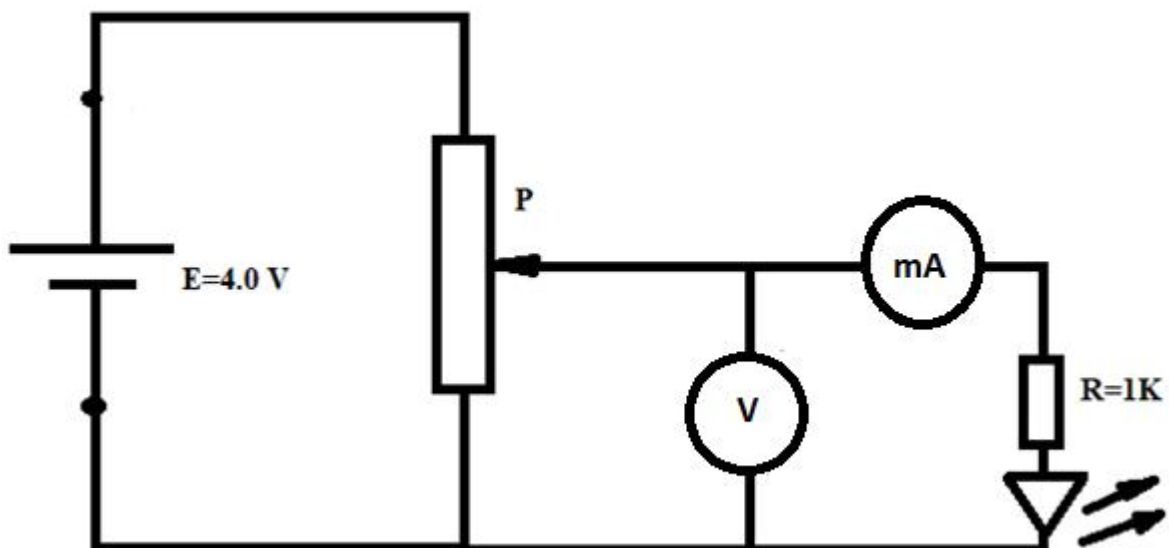


Figure 3

b. Adjust the potentiometer and complete the table below (6 marks)

V(v)	0	0.5	1.0	1.5	2.0	2.5	3.0	3.5
I(mA)								

c. Adjust the potentiometer until LED starts to glow. Record voltage_____ (1 mark)

d. Plot graph of I(mA) against V(v) (10 marks)

EXERCISE 4

Figure 4 shows a layout of a power final sub circuit. Using PVC conduit wiring system, install the circuit

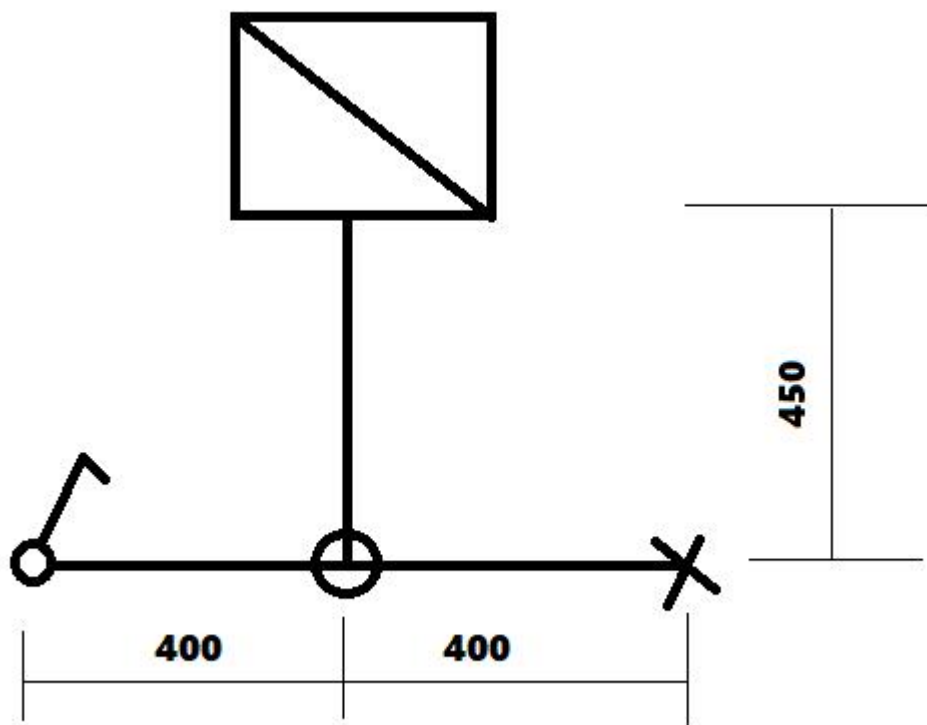


Figure 4